Travis Crumley Final Project ENGR 355 Winter Quarter 2014

Table of Contents

Introduction and Procedure

Flow Chart of Program Design

Troubleshooting

Annotated Schematic

Bill of Materials

PCB Layout

Part Information

Datasheet Locations

Introduction

This project is the final project for ENGR 355 Winter Quarter 2014 Embedded Systems Design. The project included both hardware and software elements which in combination resulted in a working board that could participate in a game known as J.S. Joust.


J.S. Joust is a relatively simple game where some music is played at a varying tempo, and depending on that tempo the players can move their game pieces faster or slower. The goal of the game is to cause the other players to move their game pieces faster than the tempo allows, causing them to lose and drop out of the game for that round.

Procedure

The project first started with an overall schematic that was built on many elements that we had been working on in labs and classwork over the course of the quarter. We then used Mentor Graphics to create an actual circuit board to carry the required parts for the schematic, using the same processor as we used in labs on a breadboard.

Once we got the circuit boards we then spent time manually placing the parts and soldering them on. As might be expected for a project with newcomers many boards did not work properly, and extensive troubleshooting was required. Some boards, such as mine, never did become fully functional and I instead partnered up to use another student's board. This process if further documented in the troubleshooting section.

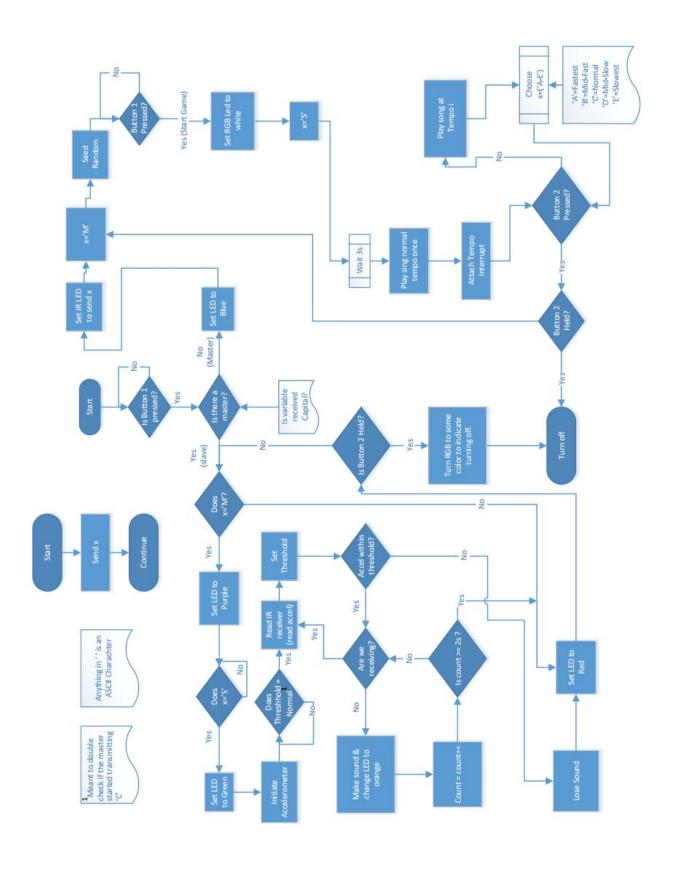The last step was to create code to actually play the game. Using the flow chart shown below, I created a master and slave portion of code that will either play music and send appropriate tempos or receive those tempos and act as a game piece—failing when the device is moved more quickly than the tempo allows.



Troubleshooting

I had several minor issues getting the initial parts and soldering many of them on by hand, but the real issues started when I plugged it into my computer. I was briefly ecstatic, as it was recognized by my computer and came up with a pop-up that said installing Generic USB Hub Driver but as nothing happened for a moment I grabbed the board and immediately yanked my hand back—the voltage regulator was extremely hot. I quickly unplugged the board and began the debug process.

The problem seemed to be related to some 3.3V connection so we first guessed that the accelerometer had a short. I used the more hardcore version of a soldering iron (with air compression) to remove it, but the pins seemed fine and that probably wasn't actually my issue. I next removed some further issues with bridging on the processor and a random wire that found its way onto my board. Testing it further I found that the jumper was also hot, and as I was testing for resistance between nodes I realized that my PMOSFET had fallen off sometime and I couldn't find it.

Isoldered on another part but realized it was the wrong one (had 1-P on it) and was starting to lose hope until Greg and Professor Tim managed to find another in the projects lab. Isoldered that on after some minor issues removing the other (who knew how hard it would be to get that little thing off—ended up removing one of its legs) and tested it again with the same overheating results. Ithen returned to trying to figure out some sort of solution testing for resistance.

We seemed to trace the resistance issue to the 3.3V line, and proceeded to take off all of my transistors in an effort to find the source of a short. Unfortunately even with that effort the short was still causing my board to heat up and I went back to the PCP Layout to see where an error might lie. I had to do quite a bit of soldering on and around the processor (and a great deal of solder-wicking) and when I saw that there were a large number of vias under the processor placed very close to the edges (and each other) the professor and I agreed that it would be wiser to work with someone else's board instead of trying to hand-solder all the tiny pins of the processor. Though it was disappointing to not get the board working I learned a great deal and since I prefer working with software it was not as frustrating as it might have been.

Since I enjoy programming the code was a relatively painless process and overall went quite well. Some challenges I had early on were solved by the group at large (namely changing 26us modulation to 2us) and the issues I did have with my code were rather quickly resolved by discussing the code and flow chart with Howie, Carlos, and Hillary in particular (as well as most of the rest of the class from time to time).


Note: Most of the "I"s in this troubleshooting process included help from the professor.


Bill of Materials

Ref I	PN	Value	Geom
C1	DK-PCC2225CT	10u	0805
C10	DK-PCC180CNCT	18p	0805
C11	DK-PCC180CNCT	18p	0805
C12	DK-PCC180CNCT	18p	0805
C13	DK-PCC180CNCT	18p	0805
C2	DK-PCC2225CT	10u	0805
C3	DK-PCC2225CT	10u	0805
C 4	DK-PCC1840CT	0.1u	0805
C 5	DK-PCC1840CT	0.1u	0805
C6	DK-PCC1840CT	0.1u	0805
C 7	DK-PCC1840CT	0.1u	0805
C8	DK-PCC1840CT	0.1u	0805
C9	DK-PCC1840CT	0.1u	0805
D1	DK-MMBD4148FSCT	SOT2	3
DS1	PN-4300H1LC-T-1.75	LED_1	Γ1.75
DS10	DK-160-1169-1	led_1	206
DS6	DK-000-0000		LED_T1.75_4lead
DS7	DK-160-1169-1	led_1	206
DS8	DK-160-1169-1	led_1	206
DS9	DK-160-1169-1	led_1	206
J1	DK-H11610CT	conn_	_musbt
J2	DK-WM6406	conn1	lx6-std100
J3	DK-S1012-03		conn1x3-std100
J4	DK-S1012-03		conn1x3-std100
J5	DK-S1012-03		conn1x3-std100
J6	DK-S2012-01		conn2x1-std100
J7	DK-S2012-01		conn2x1-std100
Q1	MI-CZT2907A	SOT2	23
Q2	MI-CZT2222A	SOT2	23
Q3	MI-CZT2222A	SOT2	23
Q4	MI-CZT2222A	SOT2	23
Q5	MI-CZT2222A	SOT2	23
Q6	MI-CZT2222A	SOT2	23
Q7	DK-BS250FCT	SOT2	3

R1	DK-P10KACT	10K	0805
R10	DK-P1KACT	1K	0805
R11	DK-P1KACT	1K	0805
R12	DK-P1KACT	1K	0805
R13	DK-P1KACT	1K	0805
R14	DK-P1KACT	1K	0805
R15	DK-P220ACT	220	0805
R16	DK-P220ACT	220	0805
R17	DK-P150ACT	150	0805
R18	DK-P33ACT	33	0805
R19	DK-P33ACT	33	0805
R2	DK-P10KACT	10K	0805
R20	DK-P20ACT	20	0805
R3	DK-P10KACT	10K	0805
R4	DK-P10KACT	10K	0805
R5	DK-P2.2KACT	2.2K	0805
R6	DK-P1KACT	1K	0805
R7	DK-P1KACT	1K	0805
R8	DK-P1KACT	1K	0805
R9	DK-P1KACT	1K	0805
S 1	MO-101-0134-EV	switch	_35X60mm
S2	MO-652-STSM-31-N	switch	_35X60mm
S3	MO-652-STSM-31-N	switch	_35X60mm
U1	DK-MMA8452QR1CT	qfn_1	6_mma
U2	DK-568-8521		sqfp_7x7_48
U3	DK-LM1117MP-3.3CT	3.3	rlp230
X1	DK-887-1121-1	12.0M	Hz xtal_smd_7m

PCP Layout

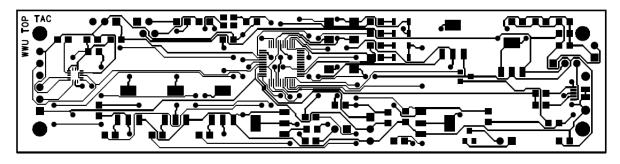

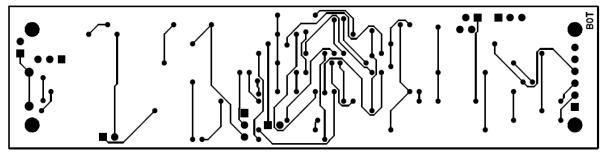

C1 to C3 - 10u Capacitor

Part #: PCC2225CT

Purchasing Source: Digikey Price: Similar Items Cost \$0.1

Function:

C1 is used as a decoupling capacitor.

C2 and C3 are used to support the voltage regulator

Datasheet Name: Capacitor



Package: 0805 (2012 Metric)

Mentor Graphics Location: Capacitor -> 0805 Cer SMD

C4 to C9 - 0.1u Capacitor

Part #: PCC1840CT

Purchasing Source: Digikey Price: Similar Items Cost \$0.1

Function: C4 and C5 are used as decoupling capacitors

C6 is connected from 3.3V to ground to help the IR Reciever

C7 and C8 assist the Accelerometer

C9 with R2 forms a debounce circuit for the Reset function

Datasheet Name: Capacitor



Package: 0805 (2012 Metric)

Mentor Graphics Location: Capacitor -> 0805 Cer SMD

C10 to C13 - 18pF Capacitor

Part #: PCC180CNCT

Purchasing Source: Digikey Price: Similar Items Cost \$0.1

Function:

C10 and C11 filter the input/output of the crystal

C12 and C13 with R18 and R19 form a low pass filter to remove noise on

the USB data wires

Datasheet Name: Capacitor



Package: 0805 (2012 Metric)

Mentor Graphics Location: Capacitor -> 0805 Cer SMD

D1 - Diode

Part #: MMBD4148FSCT-ND Purchasing Source: Digikey

Price: \$0.19

Function: Diode used to support the Speaker


Datasheet Name: Diode




Package: TO-236-3, SC-59, SOT-23-3

Mentor Graphics Location:

Active Discrete -> WWU Diode -> Diode MMBD4148 -> SOT23

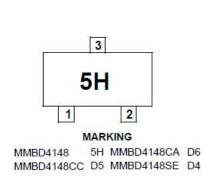

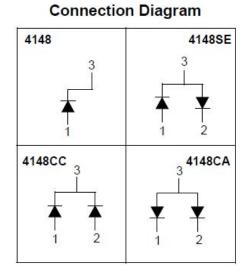

DS1 - IR LED

For more Information, see IR LED near the end of the part information section

Mentor Graphics Location:

Active Discrete -> WWU Diode -> Diode MMBD4148 -> SOT23

DS6 - RGB LED

Part #: 754-1615-ND

Purchasing Source: Digikey

Price: \$1.89

Function: We use this RGB LED to tell the player if the device is ready


and game results

Datasheet Name: RGB LED



Package: Radial - 4 Leads Mentor Graphics Location:

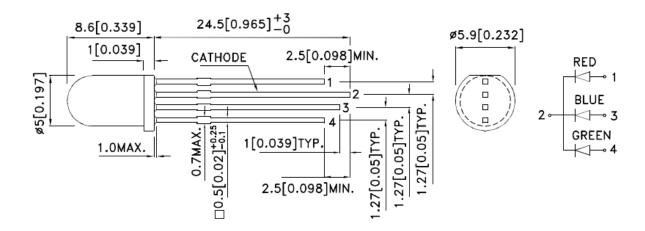Active Discrete -> WWU LED -> Common Anode -> RGB Led refine



DS7 to DS10 - Indicator LEDs

Part #: 160-1169-1

Purchasing Source: Digikey

Price: \$0.34

Function: An Indicator LED for debugging and other uses

Datasheet Name: Indicator LED



Package: 1206 (3216 Metric) Mentor Graphics Location: N/A J1 - Micro USB Connector

Part #: H11610CT

Purchasing Source: Digikey

Price: \$1.18

Function: This allows the circuit to be programmed/powered by a

computer


Datasheet Name: Micro USB



Package: ZX62D-B-5P8

Mentor Graphics Location: Other -> Connector: Micro USB -> Only Refine

option

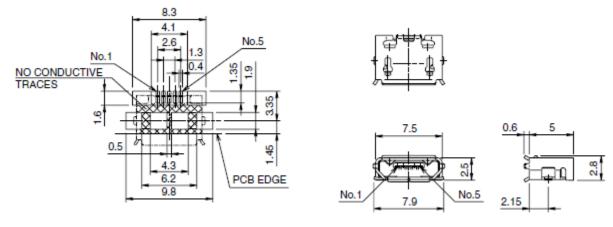

J2 - 1x6 Header Pins

Part #: WM6406

Purchasing Source: Digikey

Price: \$0.29

Function: Header Pins for Input/Output (not actually used in circuit) here

for possible need for debugging/fixing errors

Datasheet Name: 1x6 Header



Package: 0022284060

Mentor Graphics Location: N/A

J3 to J5 - 1x3 Header Pins

Part #: S1012-03

Purchasing Source: Digikey

Price: \$0.29

Function: Header Pins for connecting lines with jumpers

Datasheet Name: 1x3 Header



Package: PTC03SAAN

Mentor Graphics Location: N/A

J6 to J7 - 2x1 Header Pins

Part #: S2012-01

Purchasing Source: Digikey

Price: \$0.54

Function: Header Pins for attaching the battery

Datasheet Name: 2x1 Header



Package: PTC01DAAN

Mentor Graphics Location: N/A

Q1 - PNP Transistor

Part #: CZT2907A from Mouser, MMBT2907A-FDITR-ND from Digikey

Purchasing Source: Digikey or Mouser

Price: \$0.02295

Function: A PNP BJT Transistor used with the IR LED of the circuit

Datasheet Name: PNP Transistor




Package: TO-236-3, SC-59, SOT-23-3

Mentor Graphics Location:

Active Discrete -> WWU PNP -> Big 2097 -> SOT223 -> Default

Top View

Pin-Out

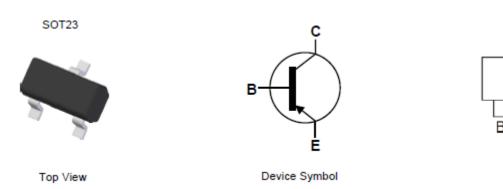

Q2 to Q6 - NPN Transistor

Part #: CZT2222A from Mouser, MMBT2222ATPMSTR-ND from Digikey

Purchasing Source: Digikey or Mouser

Price: \$0.02295

Function: A NPN BJT Transistor used with the speaker, IR LED, and RGB


LED

Datasheet Name: NPN Transistor



Package: TO-236-3, SC-59, SOT-23-3

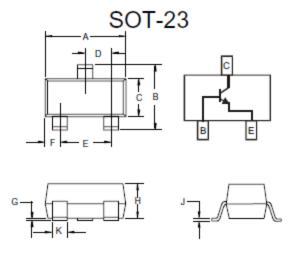Mentor Graphics Location: Active Discrete -> WWU NPN -> Big 2222A



Q7 - P Channel MOSFET

Part #: BS250FCT-ND

Purchasing Source: Digikey

Price: \$0.7


Function: A P Channel Mosfet Datasheet Name: PMosfet



Package: TO-236-3, SC-59, SOT-23-3

Mentor Graphics Location:

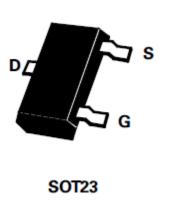Active Discrete -> WWC PMOSFET -> BS250P -> SOT-23(SMD)



R1 to R4 - 10k Resistor

Part #: P10KACT


Purchasing Source: Digikey

Price: \$0.1 Function:

R1 pulls the SA pin on the accelerometer high. This isn't strictly needed, it could just be a wire to Vcc. But if an external accelerometer was installed backwards, this limits the current to prevent frying it. R2 and C9 form a debounce circuit for the Reset function on the processor.

R3 pulls Enable function high. This function is used to enable USB programming.

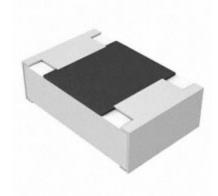R4 is a pullup for the USB Data Plus Pin. Datasheet Name: Resistor Datasheets



Package: 0805 (2012 Metric)

R5 - 2.2k Resistor Part #: P2.2KACT


Purchasing Source: Digikey

Price: \$0.1 Function:

R5 limits the current on the microprocessor pin driving the speaker to

the 4mA spec.

Datasheet Name: Resistor Datasheets

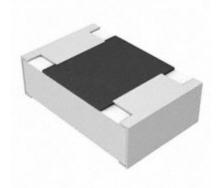

Package: 0805 (2012 Metric)

R6 to R14 - 1k Resistor

Part #: P1KACT (But only one found is P1KACCT on Website)

Purchasing Source: Digikey


Price: \$0.68 Function:

R6 and R7 Limit the current for the microprocessor pins PIO1_24 and PIO0_21 the IR LED DS1.

R8, R9, R10, R11 limit the current through the test LEDs.

R12, R13, R14 limit the current for the microprocessor pins to less than the 4mA spec. These pins drive the RGB LED.

Datasheet Name: Resistor Datasheets

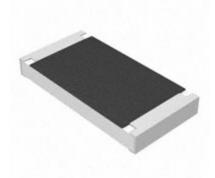

Package: 2010 (5025 Metric)

R15 to R16 - 200 Ohm Resistor

Part #: P220ACT


Purchasing Source: Digikey

Price: \$0.1 Function:

R15, R16, R17 limit the current through the RGB sections of the RGB

LED.

Datasheet Name: Resistor Datasheets

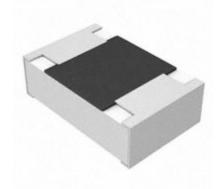

Package: 0805 (2012 Metric)

R17 - 150 Ohm Resistor

Part #: P150ACT

Purchasing Source: Digikey

Price: \$0.1 Function:

R15, R16, R17 limit the current through the RGB sections of the RGB

LED.

Datasheet Name: Resistor Datasheets



Package: 0805 (2012 Metric)

R18 to R19 - 33 Ohm Resistor

Part #: P33ACT


Purchasing Source: Digikey

Price: \$0.1 Function:

R18 & R19 with their associated capacitors C12 and C13 form a low pass

filter to remove noise on the USB data wires.

Datasheet Name: Resistor Datasheets

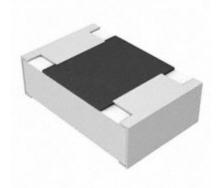

Package: 0805 (2012 Metric)

R20 - 20 Ohm Resistor


Part #: P20ACT

Purchasing Source: Digikey

Price: \$0.1 Function:

R20 limits the current through IR LED DS1.

Datasheet Name: Resistor Datasheets

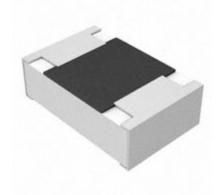

Package: 0805 (2012 Metric)

S1 - Tactile Switch


Part #: 101-0134-EV

Purchasing Source: Mouser

Price: \$0.27

Function: Tactile Switch for Input. Note: Must be used in pull-up mode.

Datasheet Name: S1 Switch

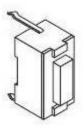

Package: N/A

Mentor Graphics Location: Other -> Switch: Pushbutton 2-pin -> MO-101

S2 to S3 - Tactile Switch Part #: 652-STSM-31-N

Purchasing Source: Mouser

Price: \$0.27

Function: Tactile Switch for Input. Note: Must be used in pull-up mode

Datasheet Name: S2 to S3 Switch



Package: STS Series - Ultraminiature Tactile Switch

Mentor Graphics Location: Other -> Switch: Pushbutton 2-pin -> MO-101

U1 - Accelerometer

Part #: MMA8452QR1CT Purchasing Source: Digikey

Price: \$1.43

Function: This is a 3 axis accelerometer that allows the circuit to detect

the orientation and degree of motion of the device.


Datasheet Name: Accelerometer



Package: 16-VFQFN

Mentor Graphics Location: Other Digital -> 12 Bit Dig Accelerometer ->

Only option

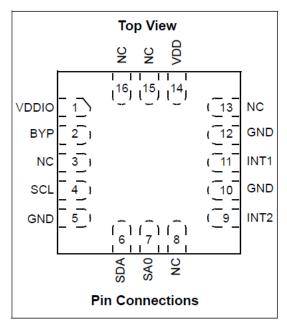

U2 - LPC11U24 Processor

Part #: 568-8521-ND

Purchasing Source: Digikey

Price: \$3.67


Function: The Main Control and Processing Unit for the circuit

Datasheet Name: Processor



Package: 48-LQFP

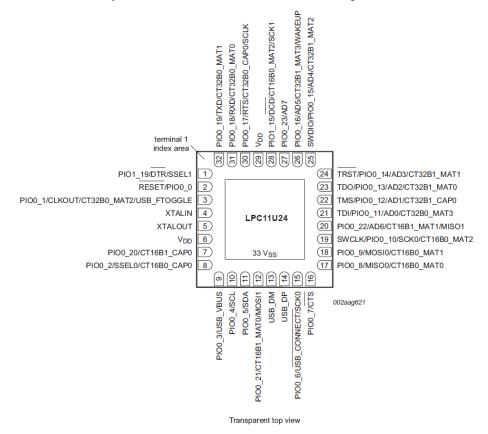Mentor Graphics Location: It's the base you start with, N/A



U3 - Voltage Regulator

Part #: LM1117MP - 3.3CT Purchasing Source: Digikey

Price: \$1.1

Function: This regulates the voltage, giving 3.3V from the a 5V source


Datasheet Name: Voltage Regulator



Package: TO-261-4, TO-261AA

Mentor Graphics Location:

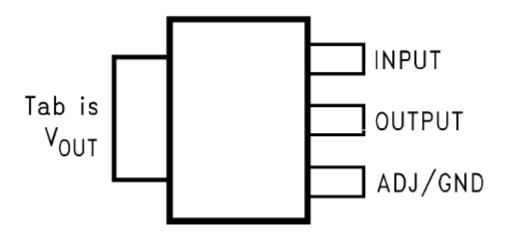Analog IC -> WWC Voltage Regulator -> List part LM 1117 -> Refine 3.3V



X1 - 12 MHz Quartz Crystal

Part #: 887-1121-1

Purchasing Source: Digikey

Price: \$0.96000

Function: This crystal serves as a clock for the circuit to base its timings off of, keeps everything in sync as von Neumann architecture requires.

Datasheet Name: 12MHz Crystal



Package: 4-SMD, No Lead (DFN, LCC)

Mentor Graphics Location: Active Discrete -> 3.2x2.5 SMD -> 12.0 MHz

IR LED

Part #: SFH4550

Purchasing Source: Digikey

Price: \$0.53

Function: This IR LED allows me to output IR signals

Datasheet Name: IR LED



Package: T13/4

Mentor Graphics Location: Represented with the following generic LED: Active Discrete -> WWU LED -> Generic LED -> 2nd option for first then only option

IR Reciever

Part #: 751-1384-5-ND

Purchasing Source: Digikey

Price: \$1.12

Function: This IR Reciever allows me to receive and interpret IR signals

Datasheet Name: IR Reciever




Package: TSOP32338 IR Reciever Module

Mentor Graphics Location: Represented with the following connector:

Other -> Connector 2-Pin -> .1 Header

Pin1 for Output, 2 for Vcc, 3 for Ground

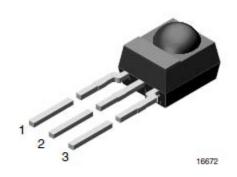

MECHANICAL DATA

Pinning for TSOP341.., TSOP343.., TSOP345..:

1 = OUT, 2 = GND, 3 = Vs

Pinning for TSOP321.., TSOP323.., TSOP325..:

1 = OUT, 2 = V_S, 3 = GND

.1" Jumper

Part #: 3M9580-ND

Purchasing Source: Digikey

Price: \$0.1

Function: This is a simple .1" Shunt Jumper

Datasheet Name: Jumper .1



Package: 3M Shunt 969 Series

Mentor Graphics Location: Other -> Connector:2x1

AAA Battery Case

Part #: BH24AAAW-ND

Purchasing Source: Digikey

Price: \$1.45

Function: Holds the mobile power source (in this case AAA batteries)

Datasheet Name: Battery Case



Package: Memory Protection Devices Inc BH24AAAW

Mentor Graphics Location: Battery is represented as a jumper

Speaker

Part #: 668-1231-ND

Purchasing Source: Digikey

Price: \$3.85

Function: The Speaker to output music if the device is a master

Datasheet Name: Speaker



Package: SPEAKER 80HM 1W 80DB28MM

Mentor Graphics Location:

Represented with: Other -> Connector 2-Pin -> .1 Header

SPST Switch

Part #: 450-2038-1-ND

Purchasing Source: Digikey

Price: \$0.16

Function: A tactile switch for input purposes

Datasheet Name: SPST Switch



Package: SWITCH TACTILE SPST-NO 0.05A 12V

Mentor Graphics Location: Other -> Switch: Pushbutton 2-pin -> MO-101